

Sophomore Circuits Lab: Lab 6: Op Amps

Author: Nathan Phipps

Group: Nathan Phipps, Anthony Stehr, Erich Wanzek

Objectives:

In this lab we utilized Op Amps in order to better understand their functions and effects when implemented in circuits.

Conclusion / Results:

Among the types of circuits we designed, we built amplifiers such as the non-inverting amplifier, the inverting amplifier, the inverting summing amplifier, the differential amplifier and a 4 stage amplifier. From our rubric we performed a number of Pspice simulations and oscilloscope trials to examine things such as frequency vs. amplitude, and V_{out} , as well as, V_{in} over time, for each of these circuits. We found that our results matched our simulations, and that there were slight variations in numbers due to the imperfect nature of hardware. Overall, our data agreed with these simulations and, this trend can be observed when comparing our Pspice simulations to our oscilloscope images. For our r_f and r_i values in our non-inverting op amp we had a 30k resistor (r_f) and 7.5k resistor in series, additionally, there was a feedback loop. This resulted in an output that was 5 times larger. Next for our inverting amplifier, we had an r_f of 30k, and an r_i of 7.5 k. The transfer function for this amp resulted in a value – 4 times the amplitude, and phase shifted the V_{out} from the V_{in} .

The summing inverting r_f (30k), and the r_i (two 15k resistors in parallel) resulted in an amplitude – 4 times in size than the original V_{in} . Again, for the summing inverting, we once again saw a 180 degree phase shift for V_{out} from V_{in} . It was interesting to note that the waveform output as V_{out} , was, in fact, just an inversion of the a square wave and triangle wave put together (i.e. when the triangle was high the inverted sum would be go low, and when the square wave was high the V_{out} would go in the opposite direction from the input). For the differential amplifier the resistors were all 10k resulting in an r_f/r_i value of unity; this resulted in an equal amplitude for V_o and V_{in} . Finally, in part two, we used 3 cascading op amps, each fed a gain of 11k Ohms, and a final buffering op amp to achieve an output gain of 1331 V (or 11^3), to simulate a value close to the lab rubrics guideline.

The aforementioned results detail some of the data as outlined in the following report. In addition to our results from the previous section, our frequency vs. amplitude simulations matched our expectations for the circuits as well. Overall, in performing our calculations, our simulations and our hardware based trials, our understanding of Op amps, as implemented in circuits has been greatly enhanced.

Outline:

- I.) Vout and Vin Simulations for Part 1
- II.) Vout and Vin Simulations (4 Stage Amplifier) for Part 2
- III.) Frequency versus Amplitude Simulations Part 1
- IV.) Frequency versus Amplitude Simulations (4 stage Amplifier) Part 2
- V.) Oscilloscope Images (Parts 1, Parts 2)
- VI.) Transfer Functions Part 1


I.) Part 1.) Vout and Vin Simulations

Part 1.) A.) Non-Inverting Amplifier (Vout and Vin):




Part 1.) B.) Inverting Amplifier (Vout and Vin):

Gain 1

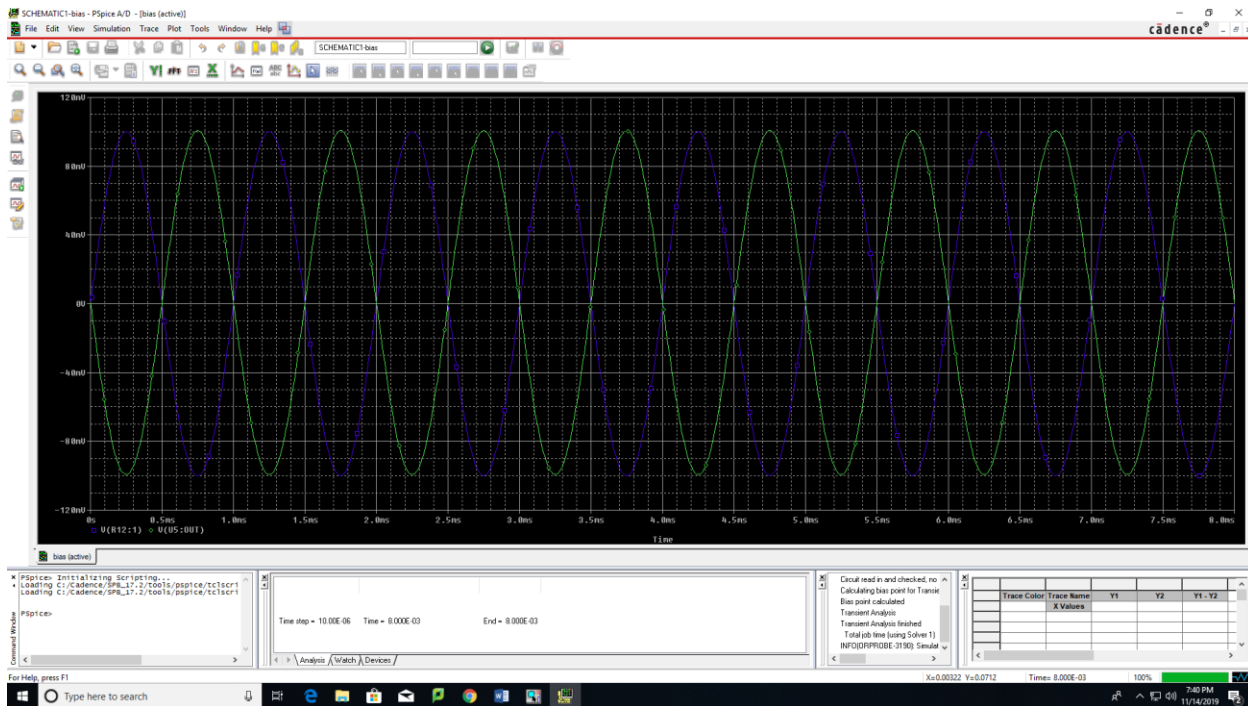


Gain 10

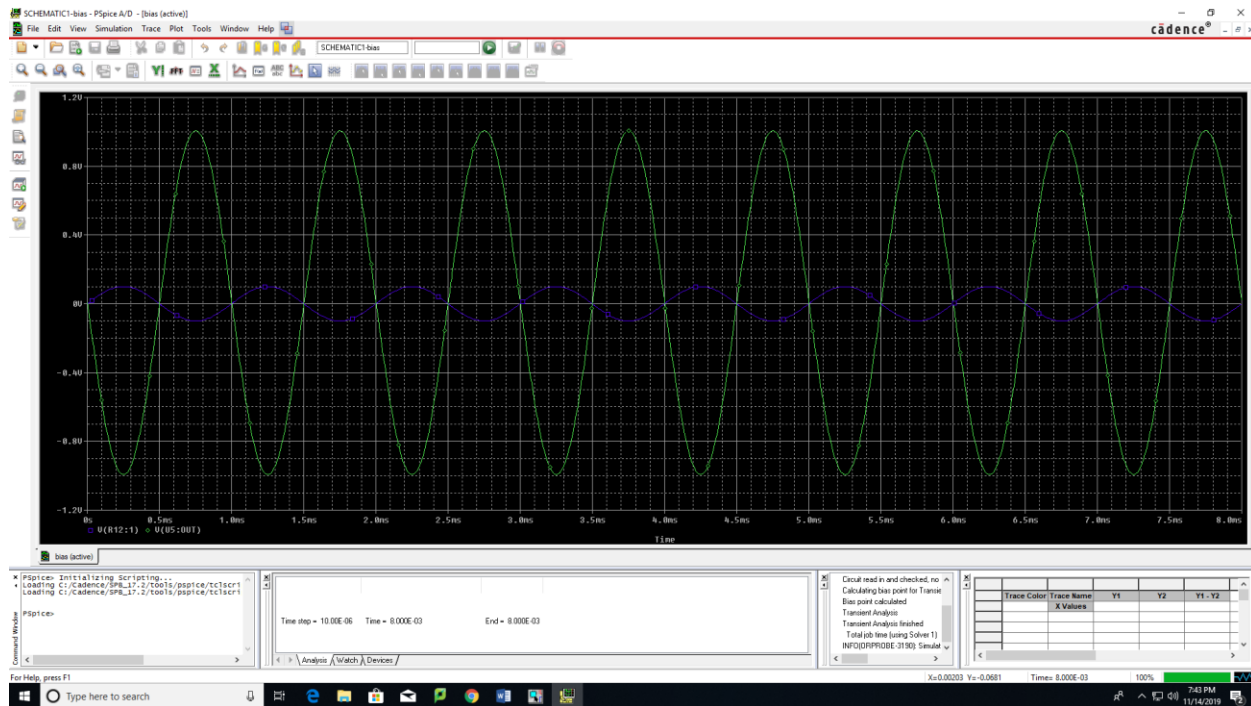


Gain 100 (increased input voltage to .2V to clip output. Rails at 18v, (.2V*100=20V) 2v over rail voltage




Part 1.) C.) Inverting Summing Amplifier (Vout and Vin):

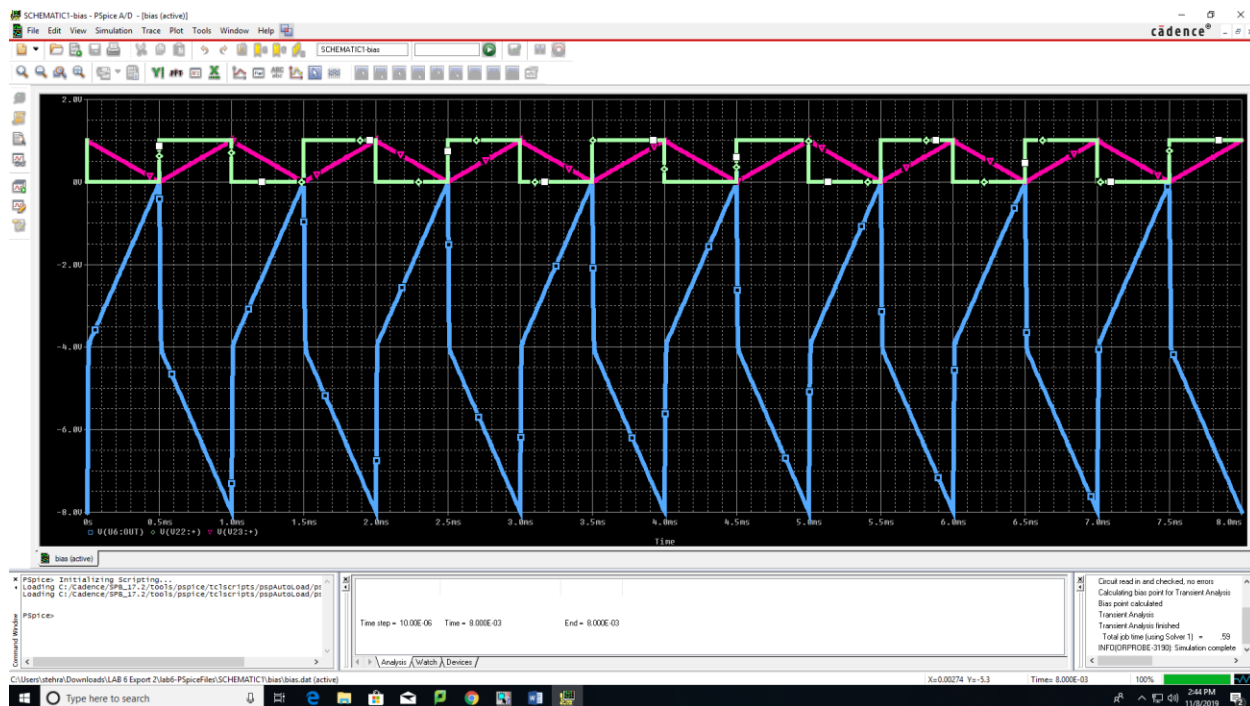

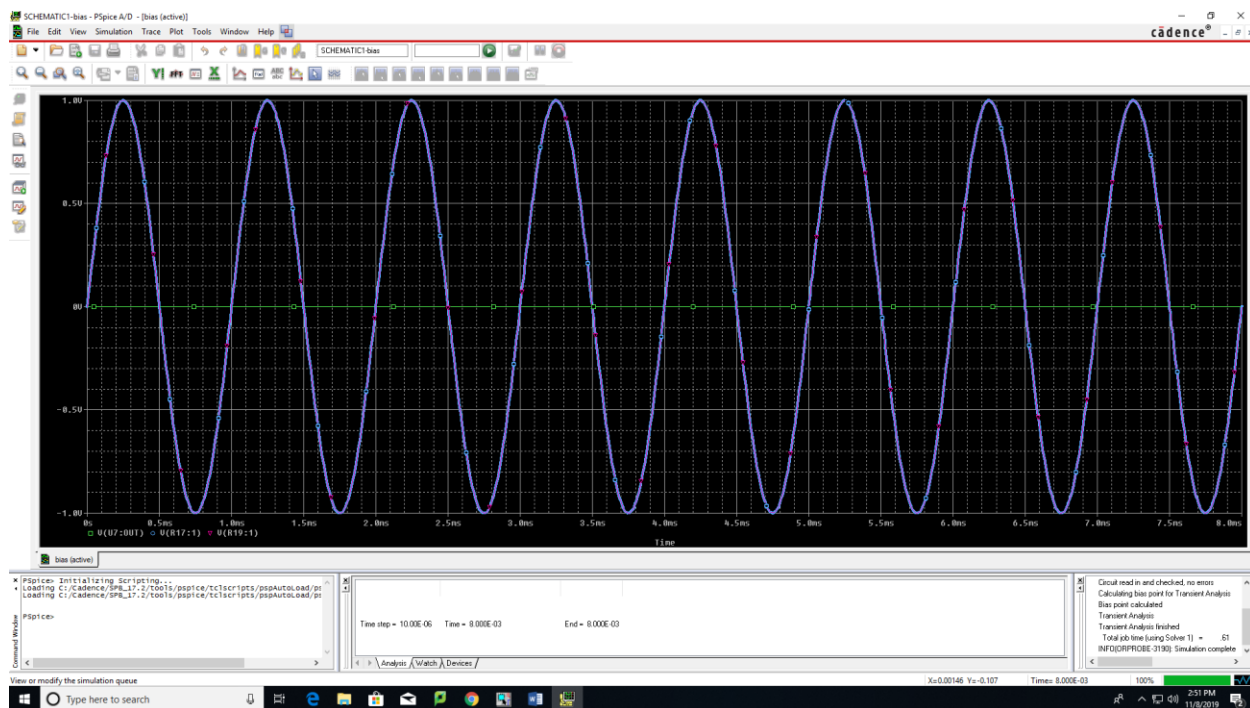Part 1.) D.) Difference Amplifier (Vout and Vin):



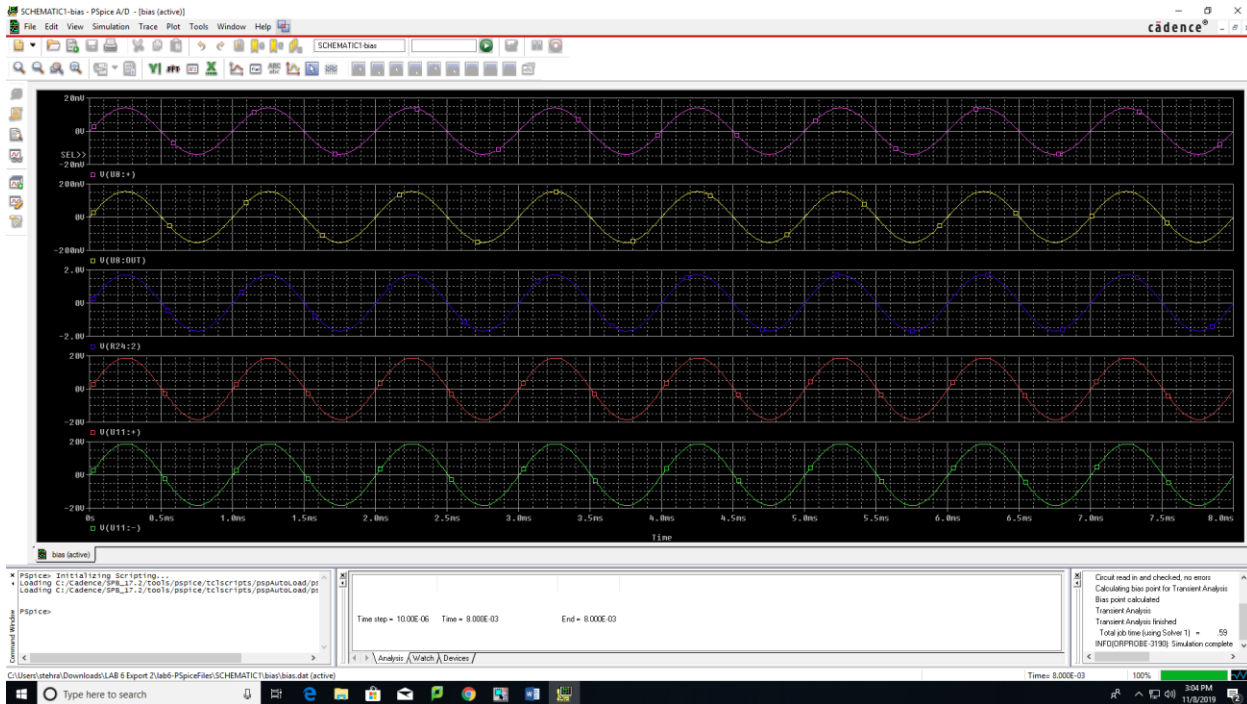
II.) Part 2.) Vout and Vin Simulations (4 Stage Amplifier)




III.) Part 1.) Frequency versus Amplitude Simulations

Part 1 A.) Frequency versus Amplitude Simulations: Non-Inverting Amplifier

Non-Inverting Amplifier Schematic:

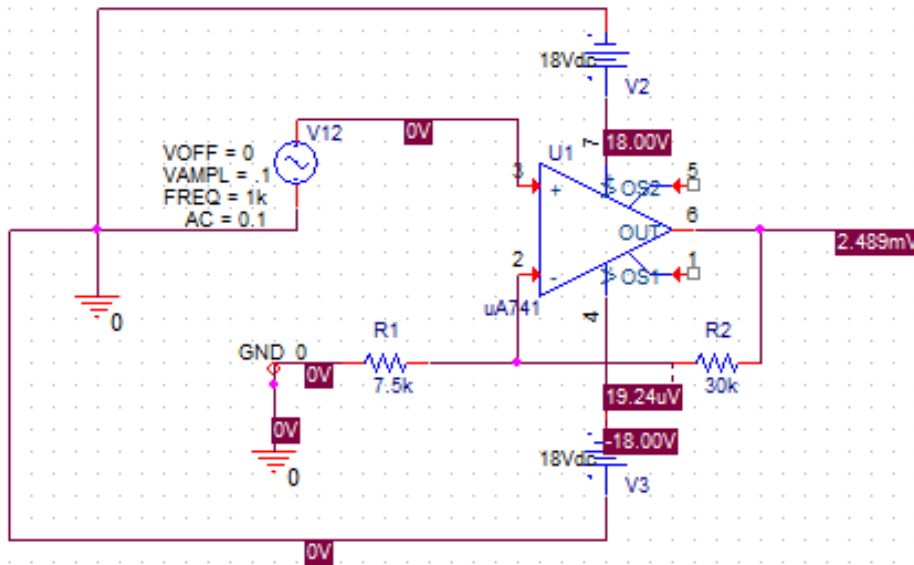


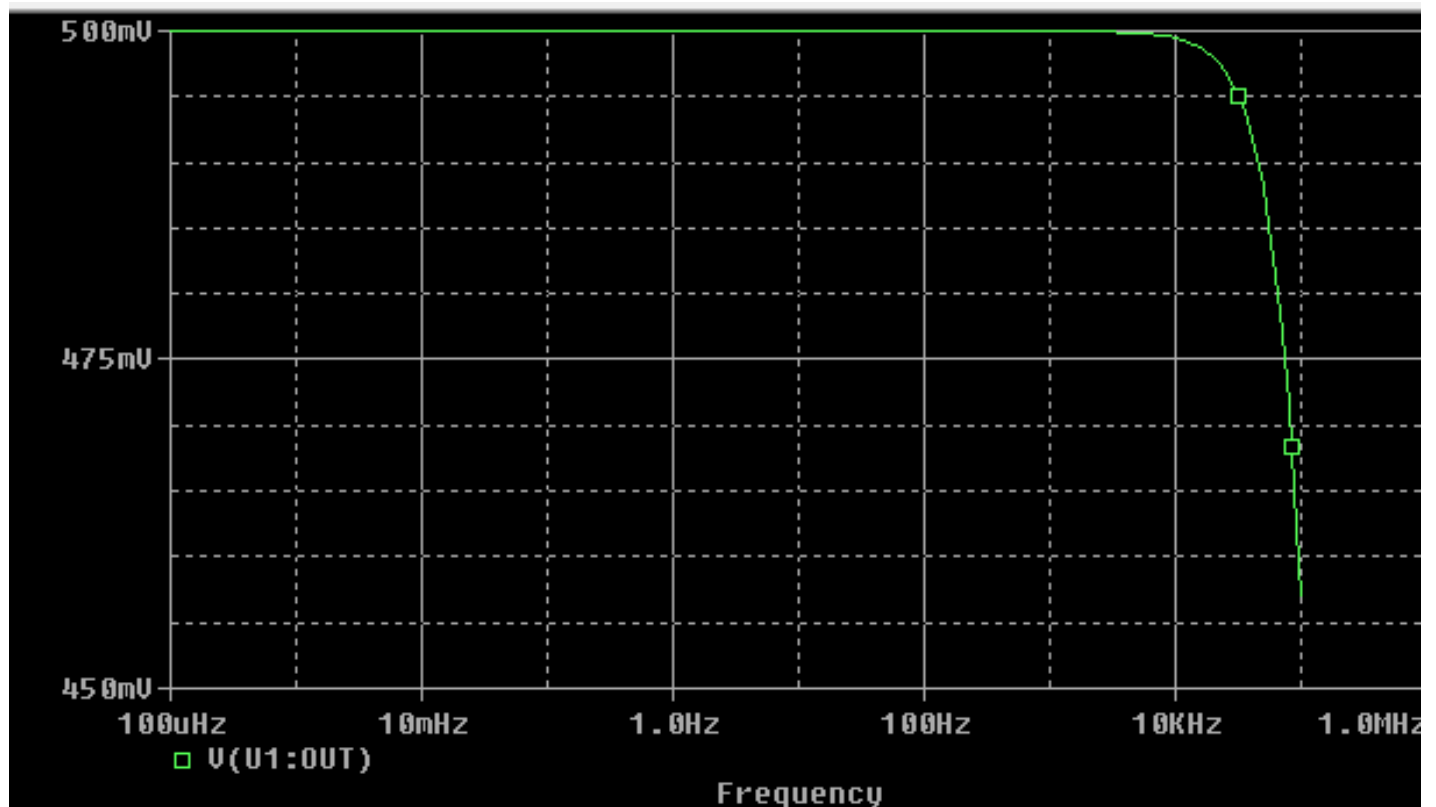Non-Inverting Simulation (Frequency versus Amplitude Simulations):




Part 1 B.) Frequency versus Amplitude: Inverting Amplifier

Inverting Amplifier Schematic:

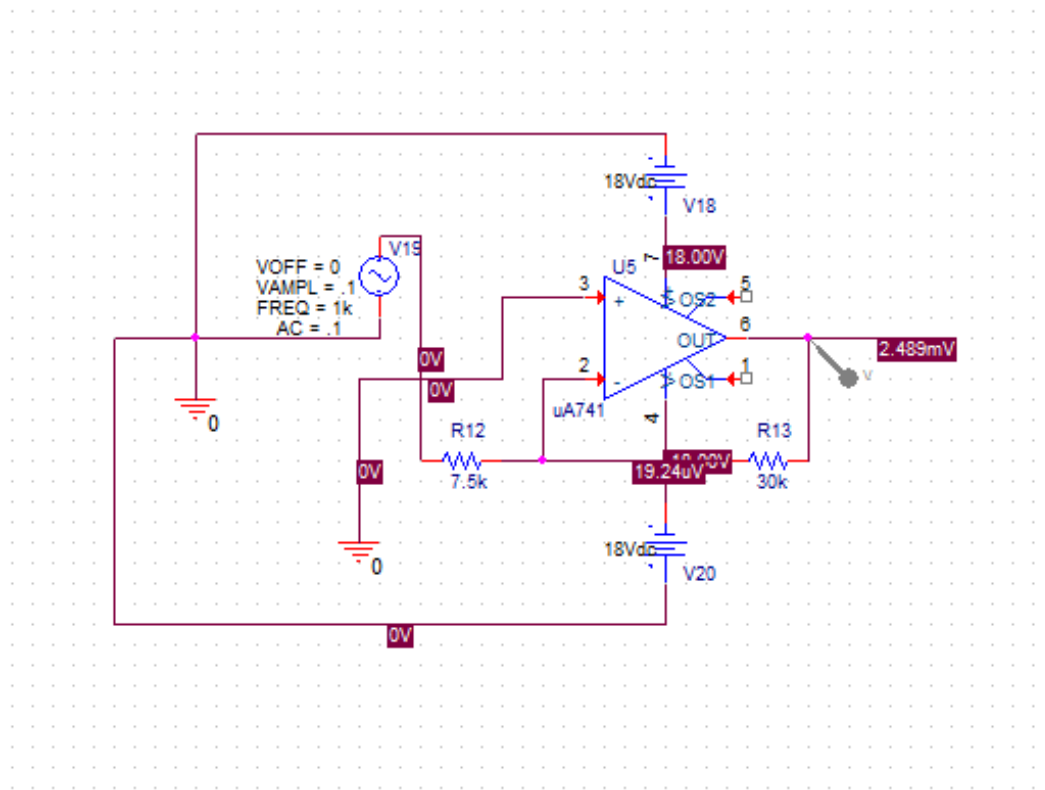


Inverting Simulation (Frequency versus Amplitude Simulations:)


Freq vs Amp Gain 1

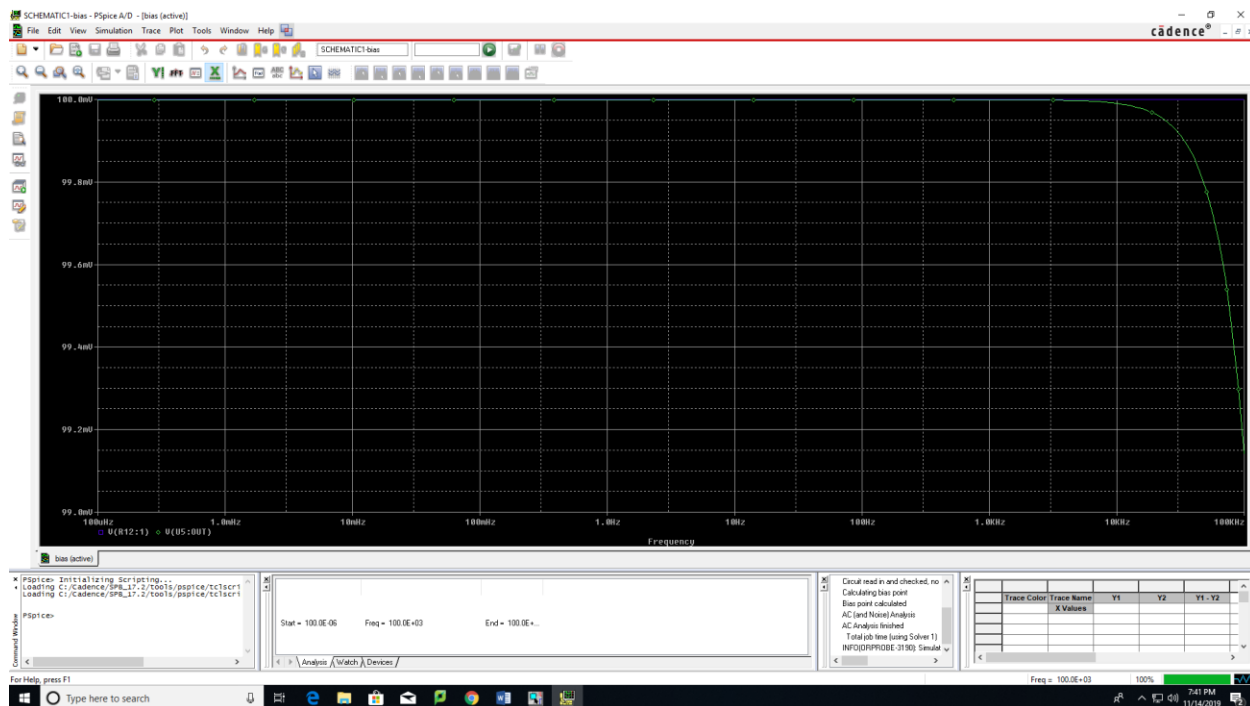

Freq vs Amp Gain 10

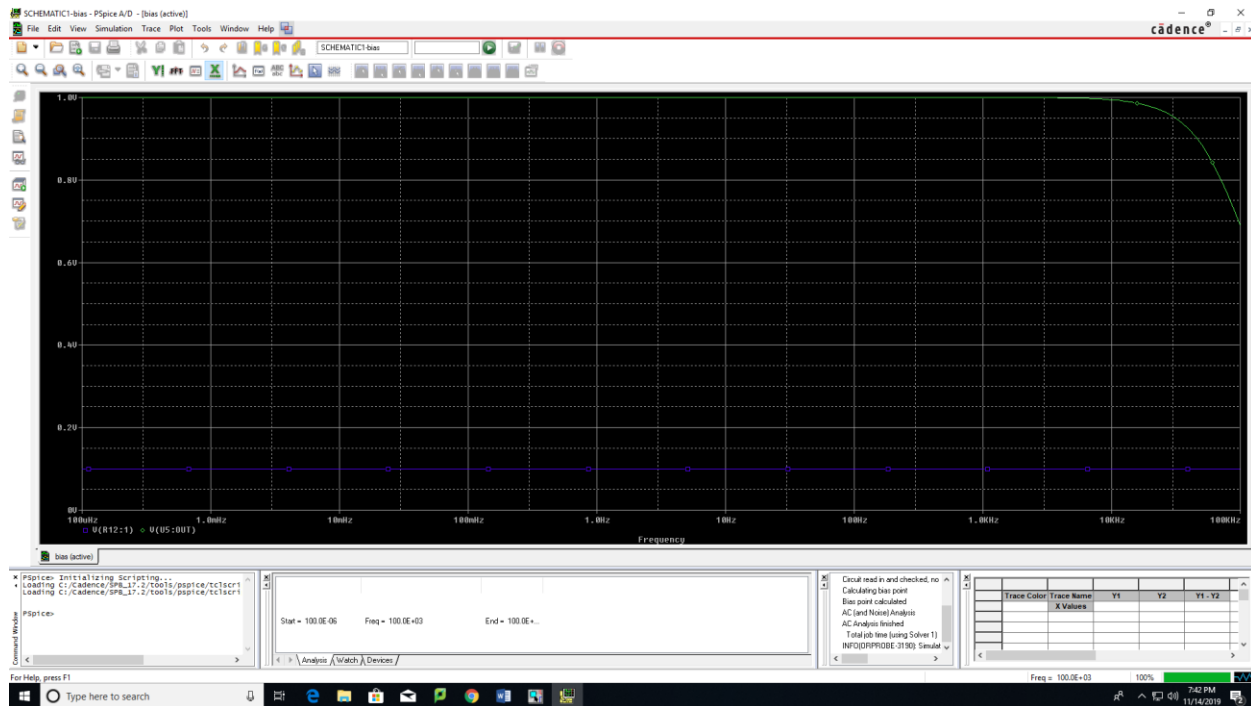


Freq vs Amp Gain 100

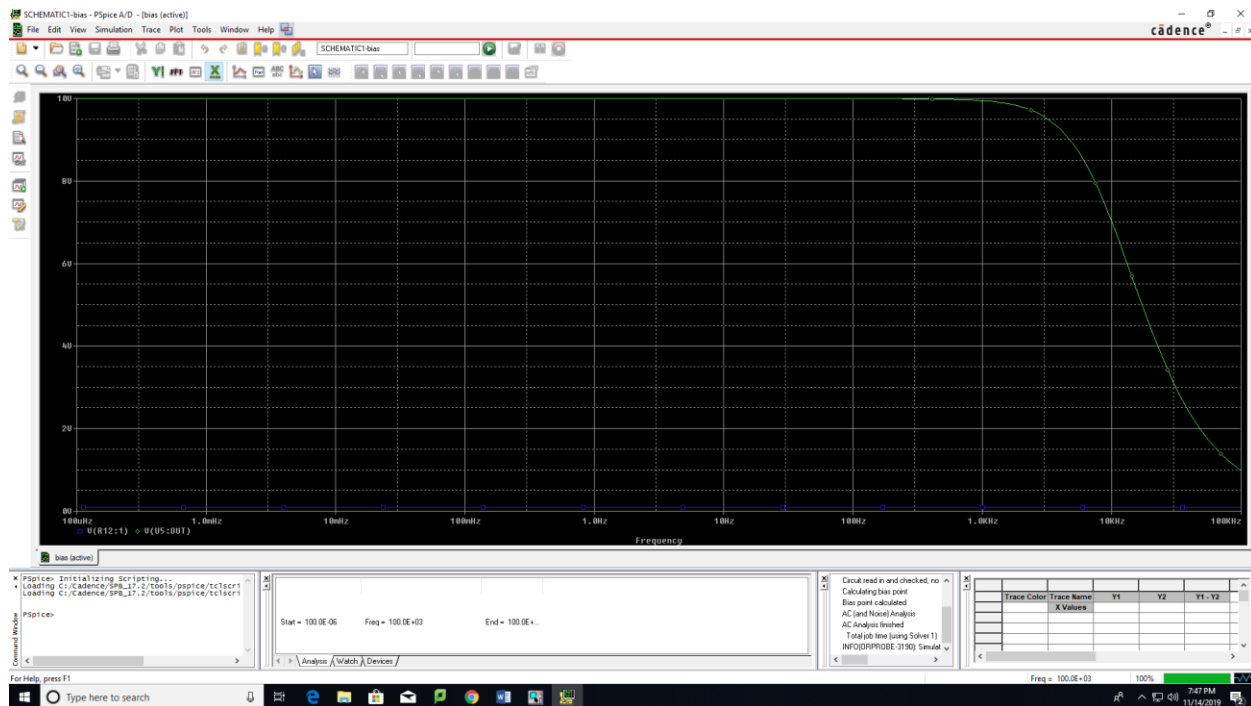


Part 1 C.) Frequency versus Amplitude Simulations: Inverting-Summing Amplifier

Inverting Summing Amplifier Schematic:

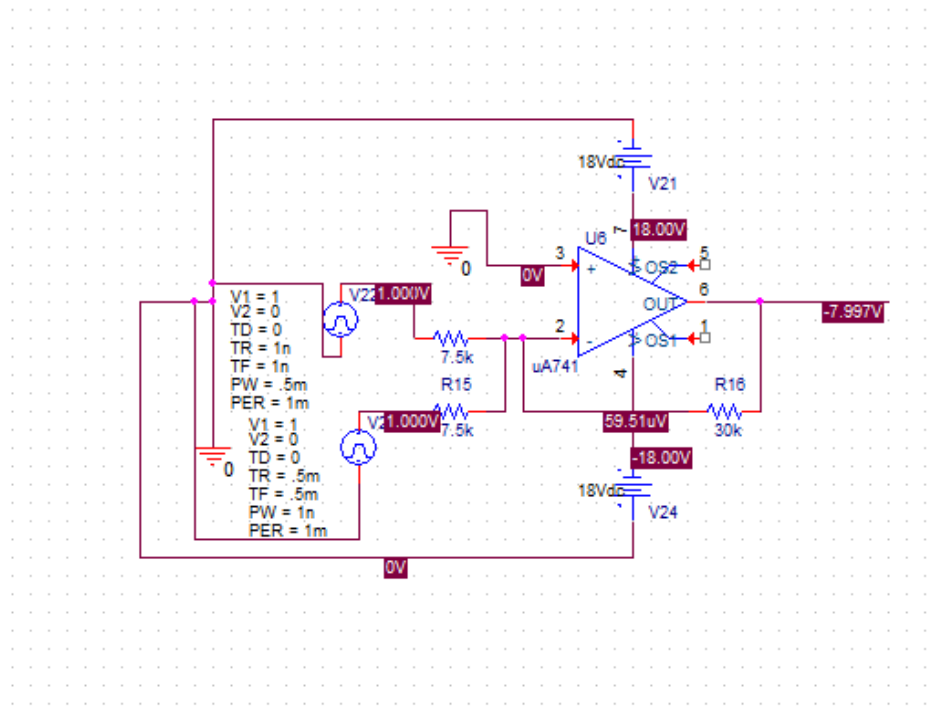


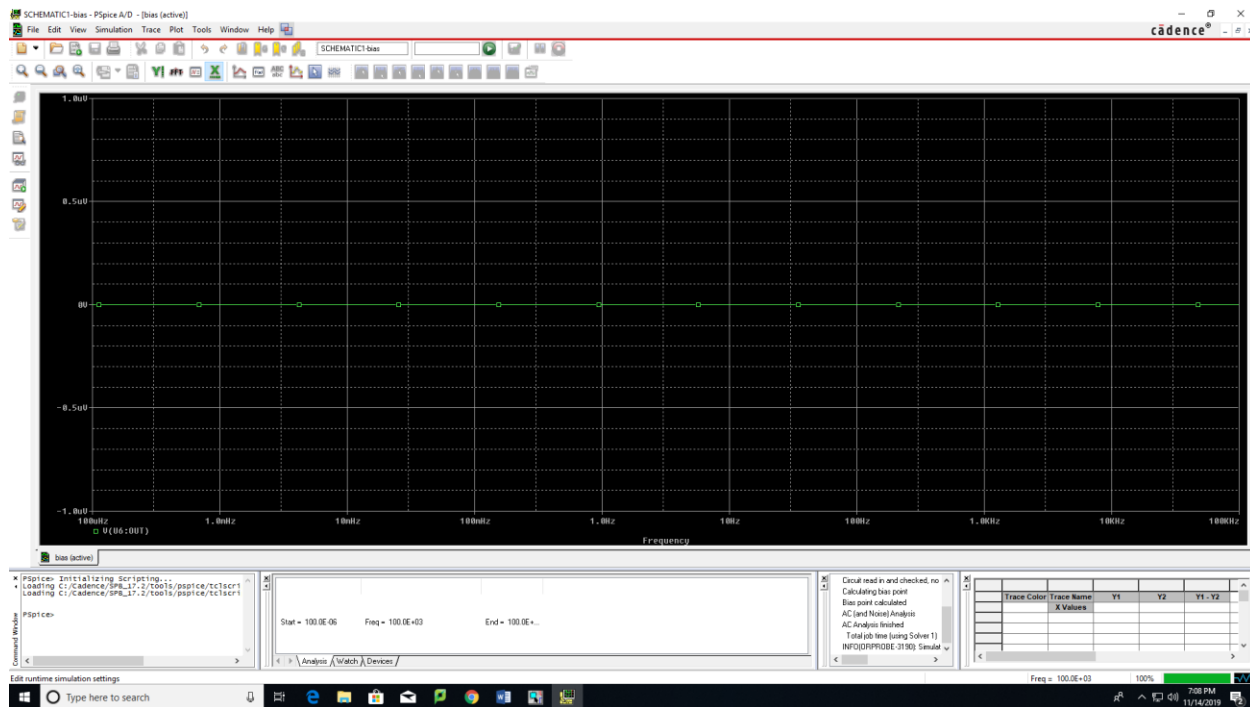Inverting Summing Amplifier (Frequency versus Amplitude Simulations):




Part 1 D.) Frequency versus Amplitude Simulations: Difference Amplifier

Difference Amplifier Schematic:

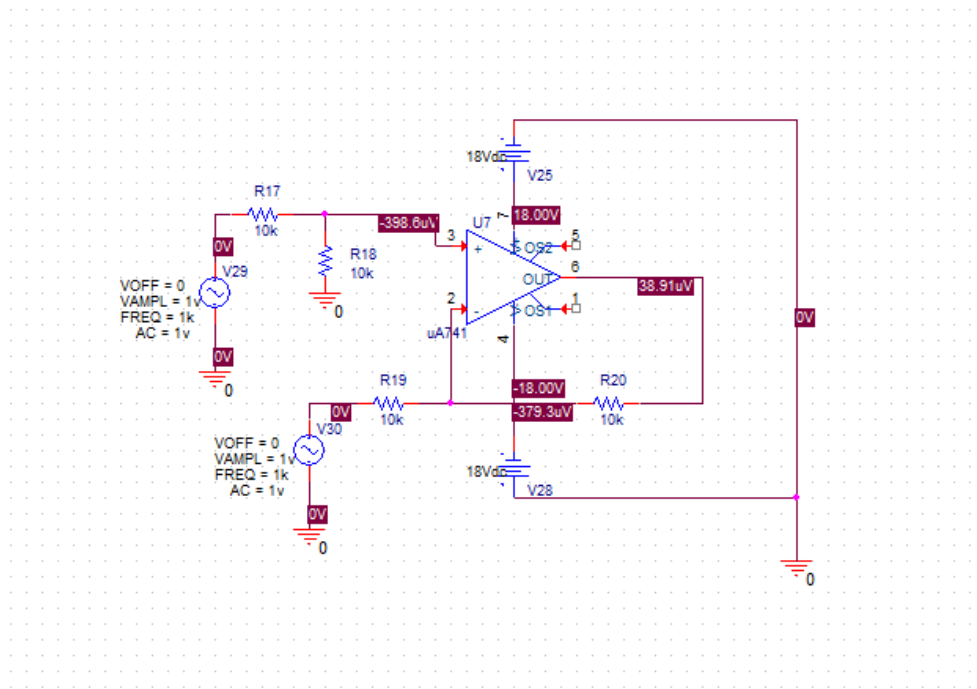

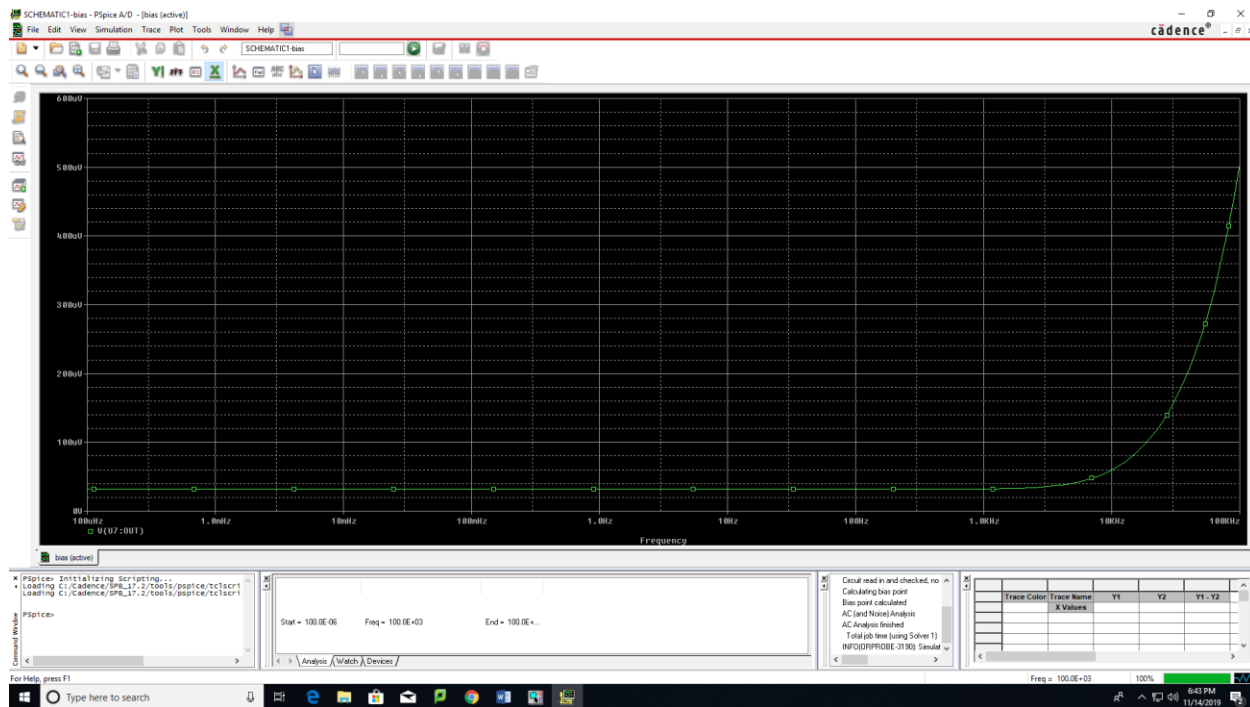Difference Amplifier Schematic (Frequency versus Amplitude Simulations):






V.) Oscilloscope Images, All Parts (Parts 1, Parts 2):


Non-Inverting Op Amp:

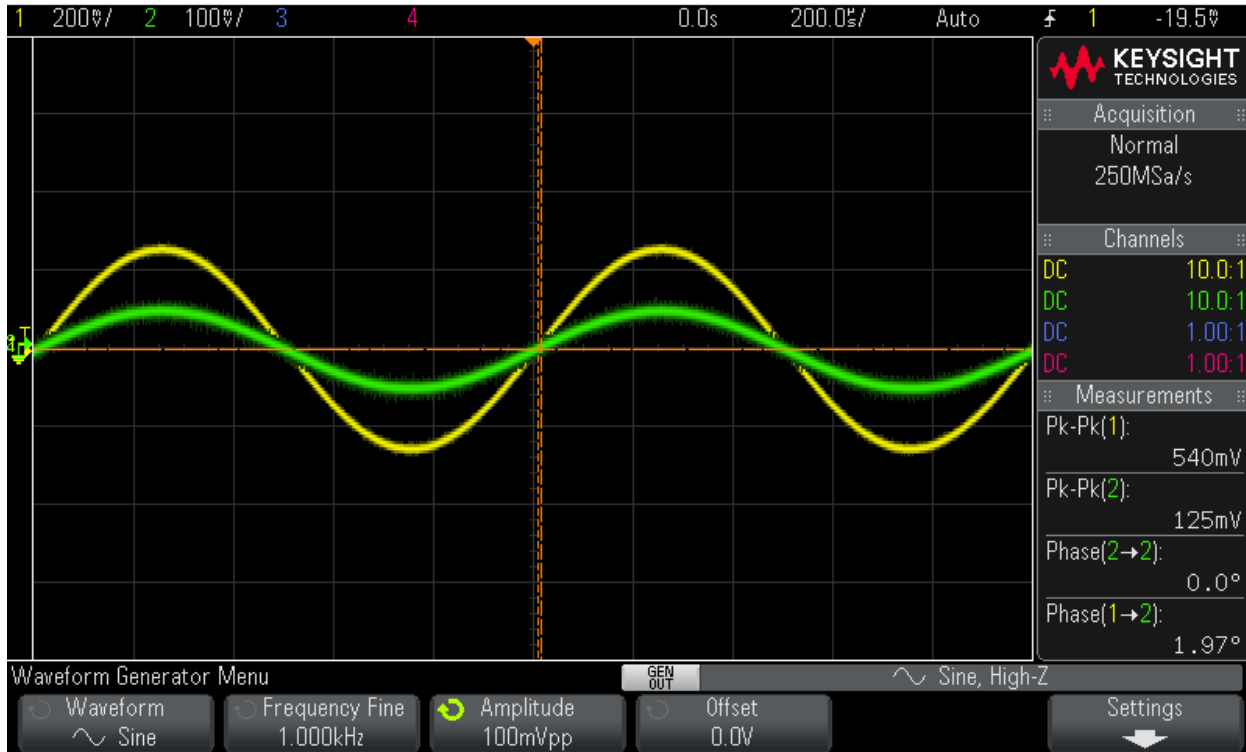DSO-X 3014A, MY54410174: Fri Oct 18 02:52:23 2019




Inverting Op Amp

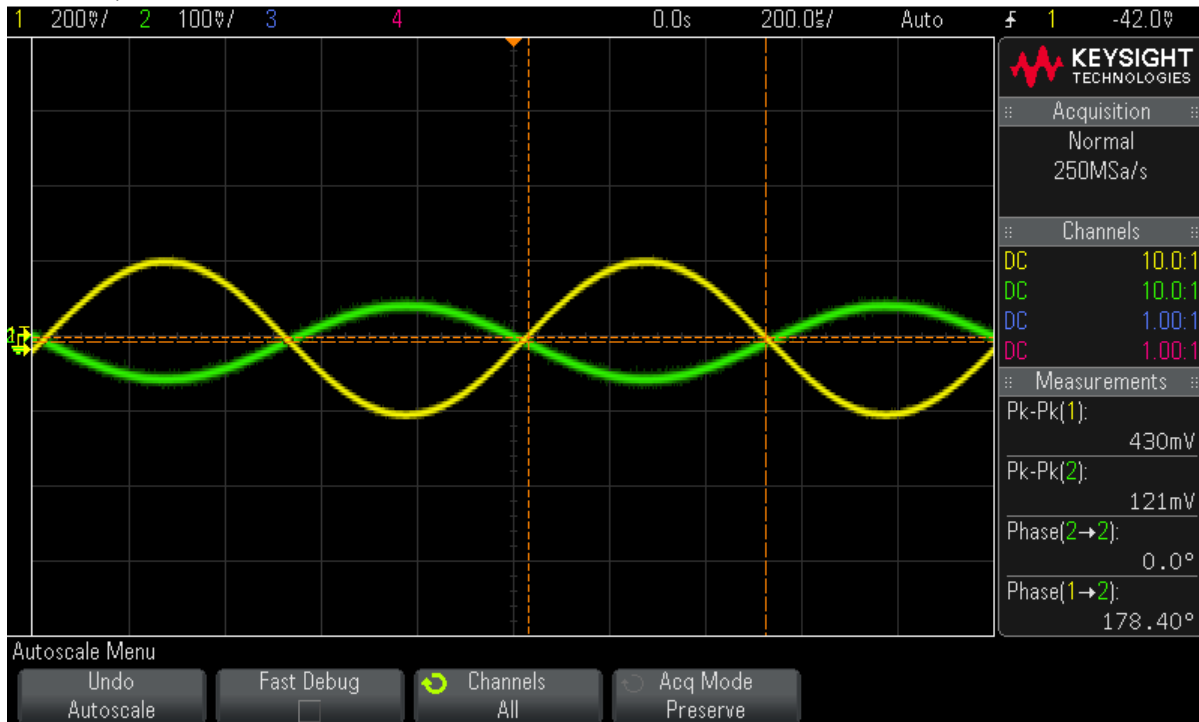DSO-X 3014A, MY54410174: Fri Oct 18 03:01:02 2019




Inverting Summing Op Amp

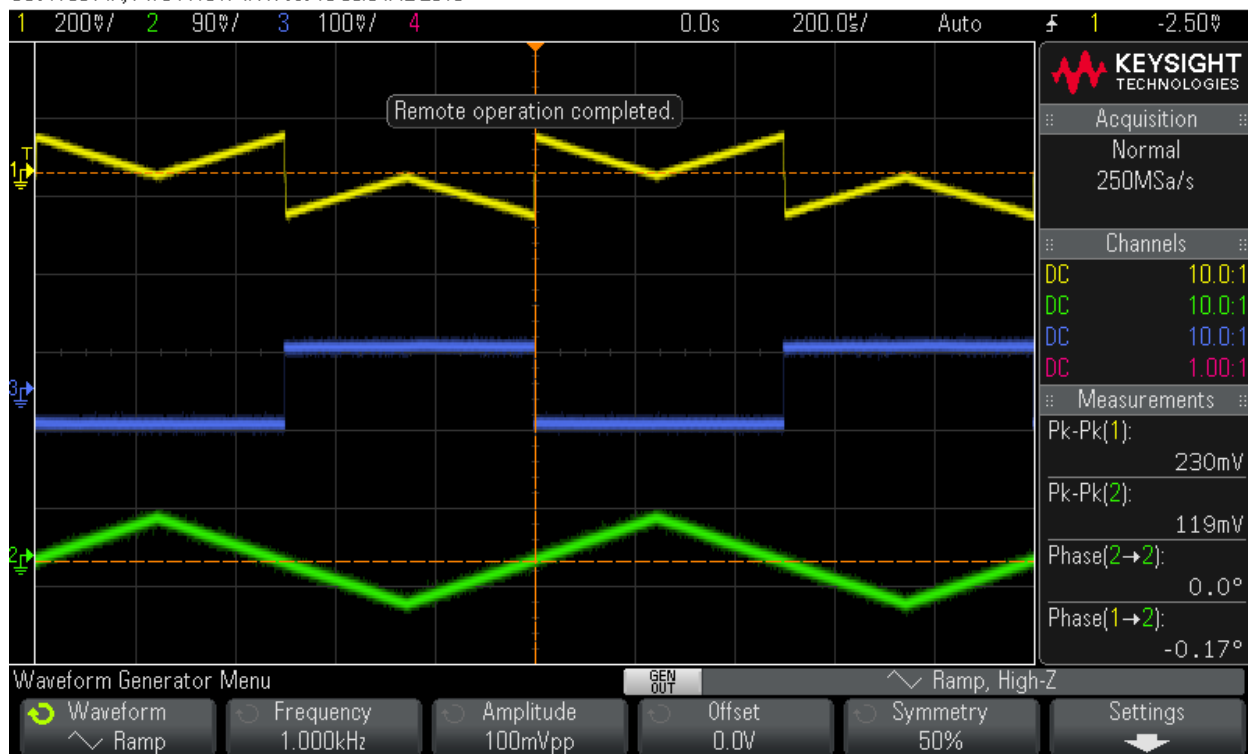DSO-X 3014A, MY54410174: Fri Oct 18 03:34:42 2019



Difference Amplifier:

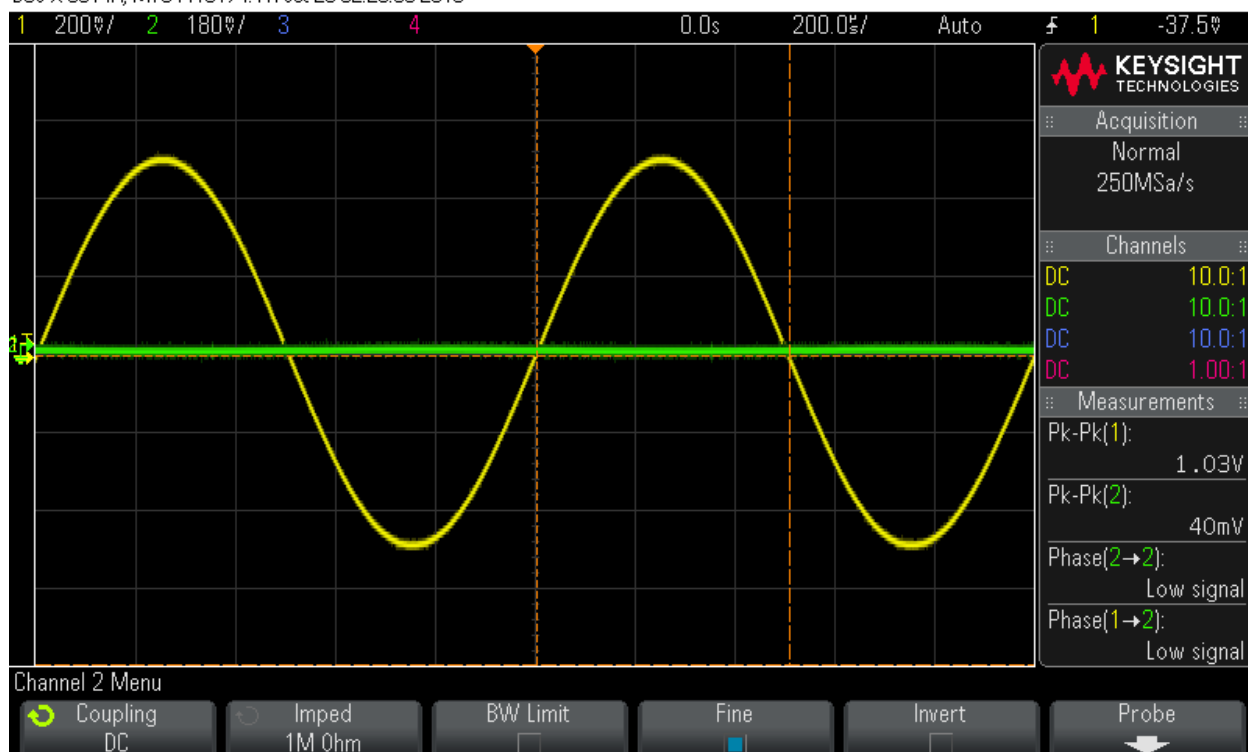DSO-X 3014A, MY54410174: Fri Oct 25 02:29:09 2019



The same difference amplifier from before, common mode rejection ratio causes cancellation from the 2sources being the same


DSO-X 3014A, MY54410174: Fri Oct 25 02:33:38 2019



4 stage amplifier 1k +10k ==11k, 1331 v output


Output Stage: 14.1mV for the four stage voltage: $(18.66/(14.1 \times 10^{-3})) = 1311.97$

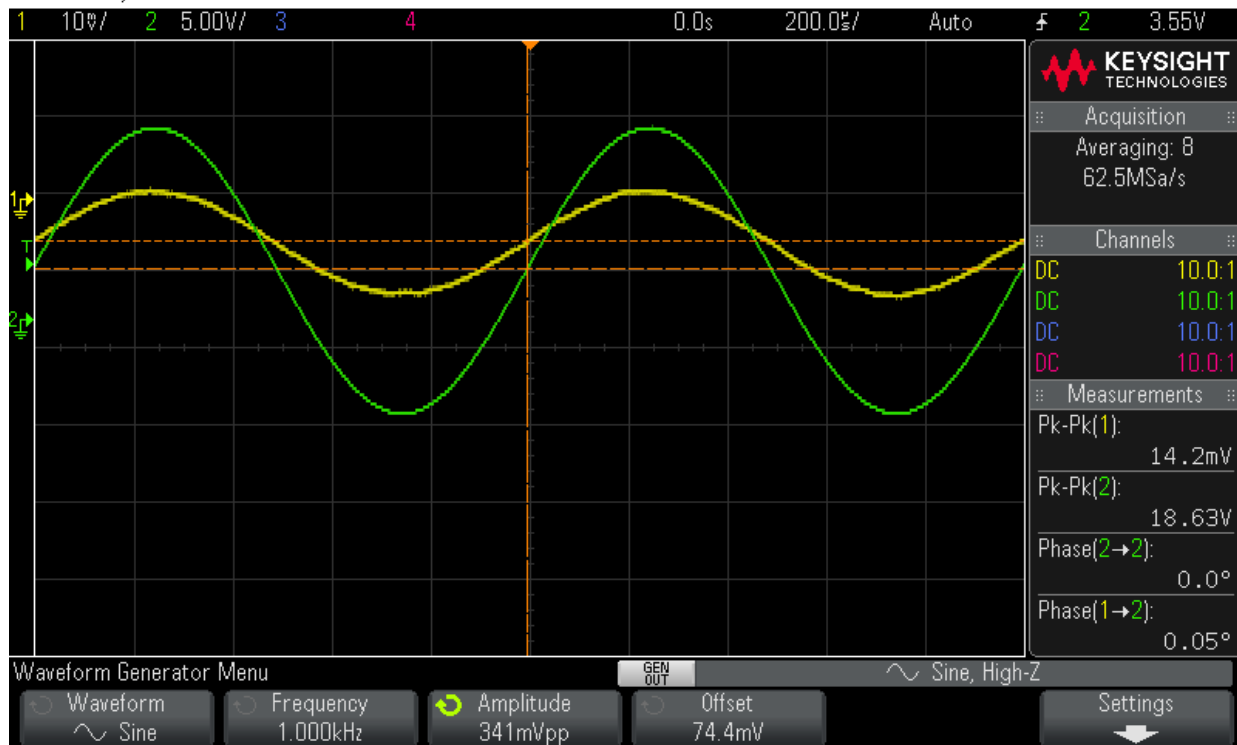DSO-X 3014A, MY54410174: Fri Nov 08 03:33:25 2019



All "Stages": Four stage Amplifier: $18.5/(14 \cdot 10^{-3}) = 1321.43$

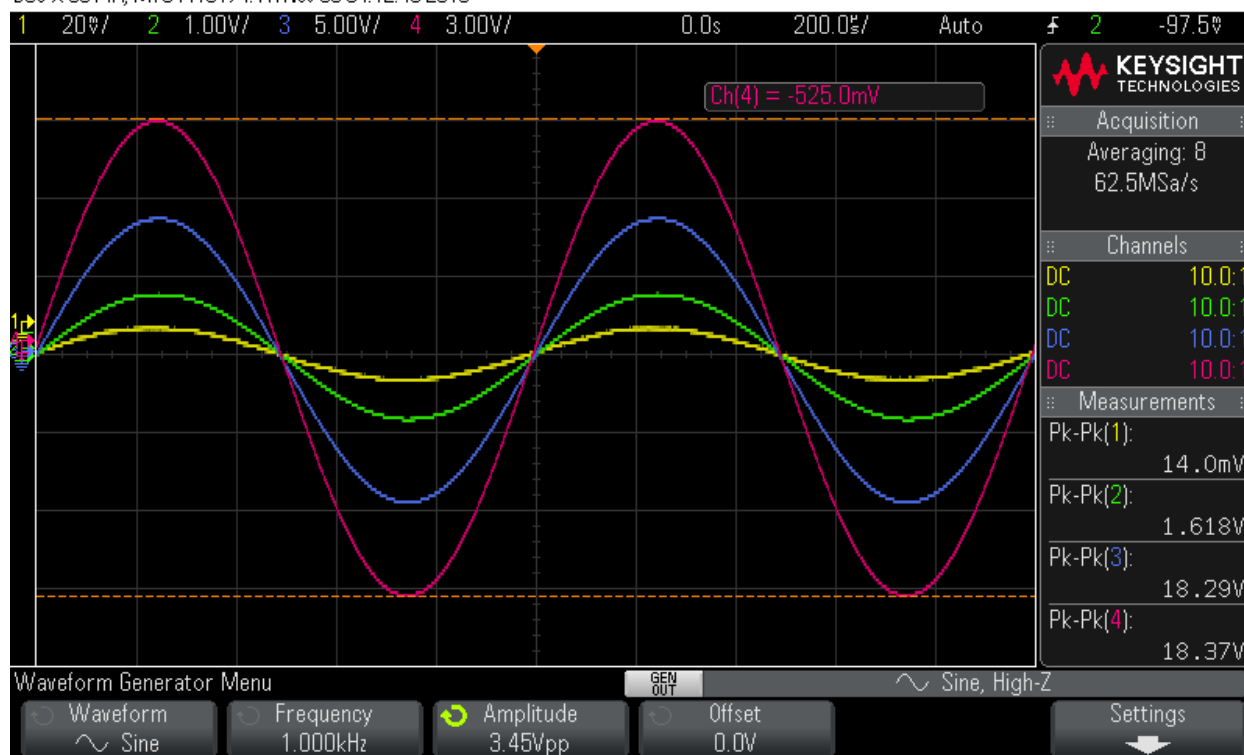DSO-X 3014A, MY54410174: Fri Nov 08 04:12:45 2019



VI.) Part 1.) Transfer Functions

Non-Inverting

$$R_f = 30k \approx 30.31k\Omega$$

$$R = 7.5k = 7.39k\Omega$$

$$A_v = 1 + \frac{30k}{7.5k} = 5$$

Inverting

$$R_f = 30k = 30.31k$$

$$R = 7.5k = 7.39k$$

$$A_v = \frac{-30k}{7.5k} = -4$$

Summing Inverted

$$R_f = 30k$$

$$R_1 = 15k$$

$$R_2 = 15k$$

$$A_v = \frac{-30k}{15k \parallel 15k} = -4$$

Differential

$$U_o = (V_{in2} - V_{in1}) \frac{R_2}{R_1}$$

$$A_v = \frac{10k}{10k} = 1$$